

Digital systems: from bits to microcontrollers

- Introduction to digital systems fundamentals
- Combinatorial digital systems
- Sequential digital systems
- Introduction to microcontrollers
- Introduction to advanced implementation platforms



LUÍS GOMES, 2014,15,16

Introduction to digital systems fundamentals

Bibliography:

Digital Logic Circuit Analysis & Design - Victor P. Nelson, H. Troy Nagle, J. David Irwin, Bill D. Carroll - Prentice Hall - ISBN 0-13-463894-8

In Portuguese:

Circuitos Digitais e Microprocessadores - Herbert Taub - McGraw-Hill - ISBN 0-07-066595-8

Alternatives:

Logic and Computer Design Fundamentals - M. Morris Mand, Charles Kime - Prentice-Hall - ISBN 0-13-182098-2

Digital Design - Principles and Practice - John F. Wakerly - Prentice-Hall - ISBN 0-13-082599-9



LUÍS GOMES, 2014,15,16

Measurement of the level of the water in a tank

Comments / suggestions ?



Measurement of the level of the water in a tank - I


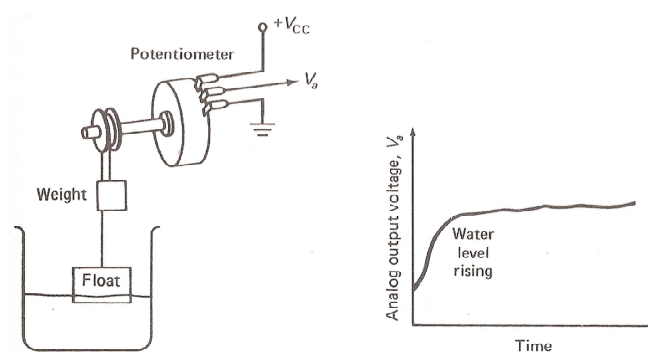


Figure from "Real-time microcomputer system design: an introduction", Peter D. Lawrence, Konrad Mauch; McGraw-Hill International Editions

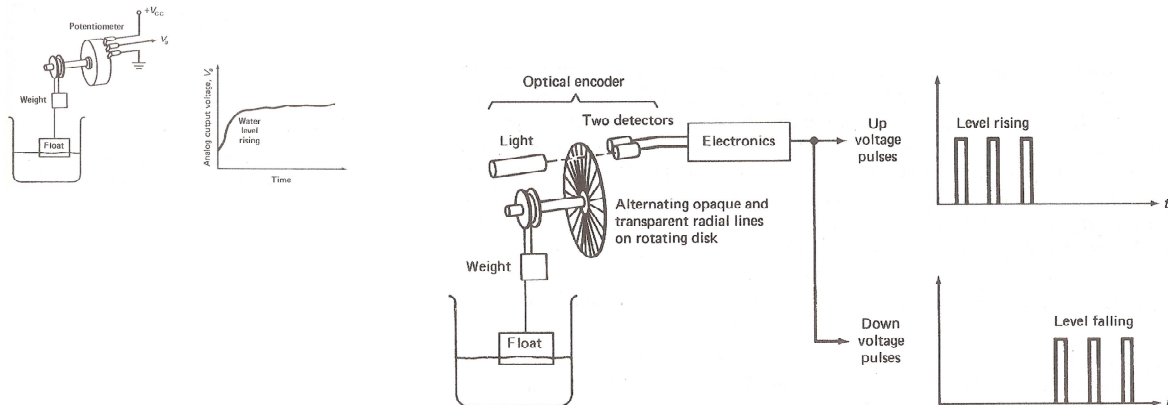Measurement of the level of the water in a tank - II




Figures from "Real-time microcomputer system design: an introduction", Peter D. Lawrence, Konrad Mauch; McGraw-Hill International Editions



LUÍS GOMES, 2014,15

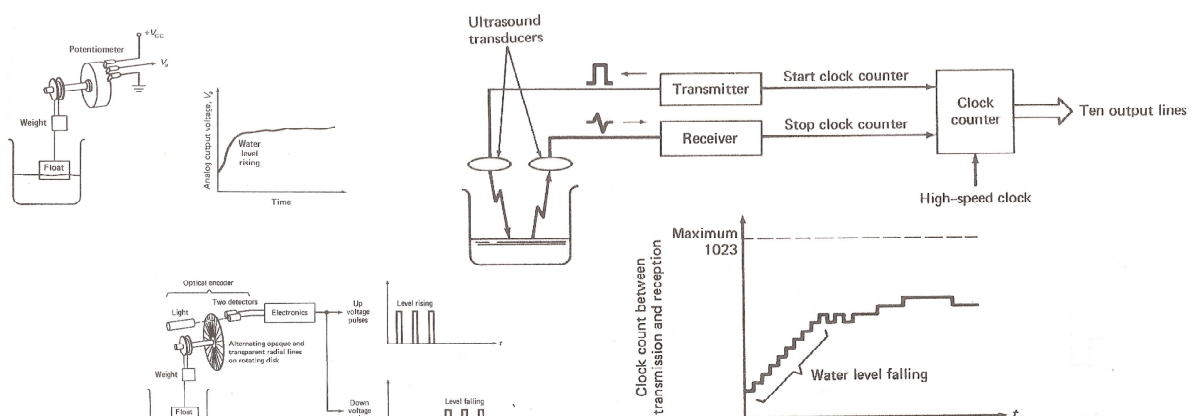Measurement of the level of the water in a tank - III






Figures from "Real-time microcomputer system design: an introduction", Peter D. Lawrence, Konrad Mauch; McGraw-Hill International Editions



LUÍS GOMES, 2014,15

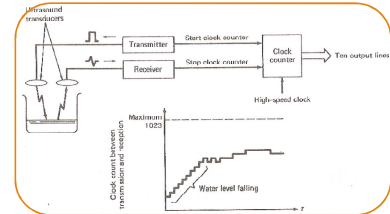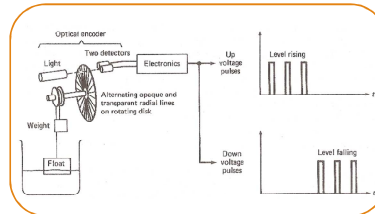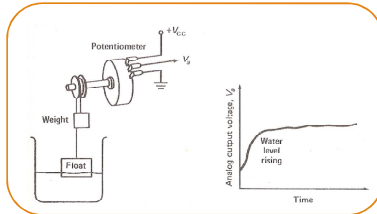Measurement of the level of the water in a tank: different types of solutions



Analog versus digital


Mechanical versus solid-state

Figures from "Real-time microcomputer system design: an introduction", Peter D. Lawrence, Konrad Mauch; McGraw-Hill International Editions



LUÍS GOMES, 2014,15

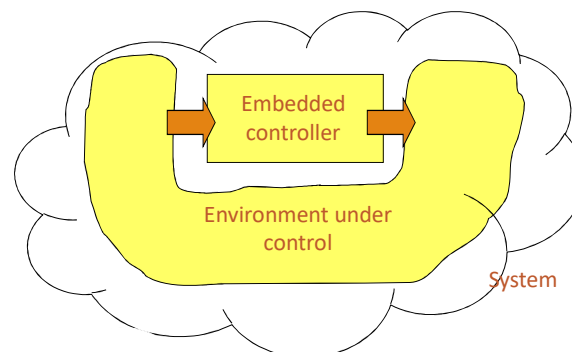Embedded controller and environment under control



LUÍS GOMES, 2014,15

Architecture of an industrial control system


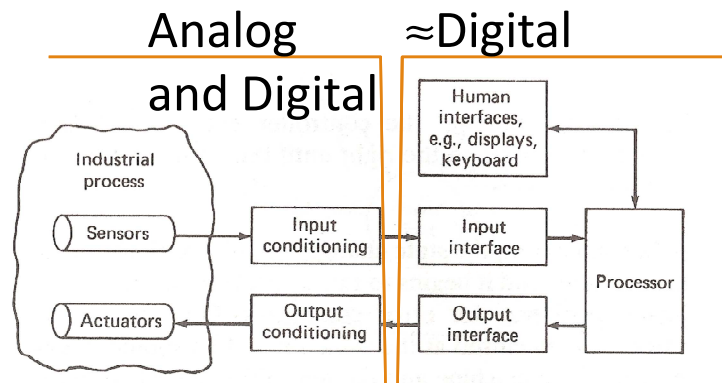


Figure adapted from "Real-time microcomputer system design: an introduction", Peter D. Lawrence, Konrad Mauch; McGraw-Hill International Editions

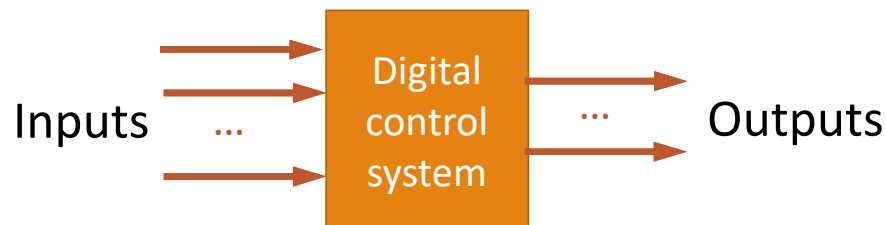Black box characterization of a digital system



Characterization of a digital system

- When outputs depend on inputs at one specific instant



Combinatorial circuits

- When outputs depend on the evolution over time of the inputs

Sequential circuits

Boolean algebra (1849)

Boolean variables can hold two truth values:

- True, False
- 1,0
- ON, OFF

Two basic operations are defined:

- OR (represented as +)
- AND (represented as .) complementing the Negation (NOT)

Boolean algebra defined over:

$$\{U = \{0, 1\}, +, \cdot\}$$

Basic postulates involving one variable

$$A + 0 = A \quad (\text{neutral})$$

$$A + 1 = 1 \quad (\text{null element})$$

$$A \cdot 1 = A$$

$$A \cdot 0 = 0$$

$$\text{Duality principle } (+ \leftrightarrow \cdot ; 0 \leftrightarrow 1)$$

$$A + A = A$$

$$A + \bar{A} = 1$$

$$A \cdot A = A$$


$$A \cdot \bar{A} = 0$$

$$A = \bar{\bar{A}} \quad (\text{involution})$$

Introducing AND function

$$K = A \cdot B$$

A	B	K
0	0	0
0	1	0
1	0	0
1	1	1

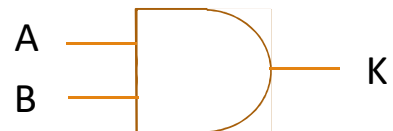

Expression


Truth table

Schematic

Introducing OR function

$$K = A + B$$

A	B	K
0	0	0
0	1	1
1	0	1
1	1	1

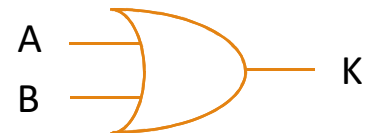

Expression

Truth table

Schematic



FACULDADE DE
CIÊNCIAS E TECNOLOGIA
UNIVERSIDADE NOVA DE LISBOA



CTS - Centre of Technology and Systems




LUÍS GOMES, 2014,15

Introducing NOT function

$$K = \overline{A}$$

A	K
0	1
1	0

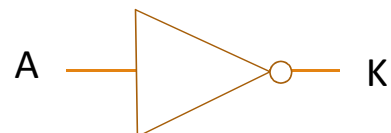

Expression

Truth table

Schematic



FACULDADE DE
CIÊNCIAS E TECNOLOGIA
UNIVERSIDADE NOVA DE LISBOA



CTS - Centre of Technology and Systems




LUÍS GOMES, 2014,15

Introducing NAND function

$$K = \overline{A \cdot B}$$

A	B	K
0	0	1
0	1	1
1	0	1
1	1	0

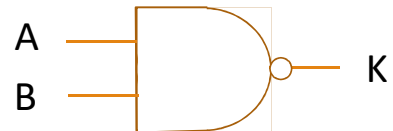

Expression

Truth table

Schematic



FACULDADE DE
CIÊNCIAS E TECNOLOGIA
UNIVERSIDADE NOVA DE LISBOA



CTS - Centre of Technology and Systems




LUÍS GOMES, 2014,15

Introducing NOR function

$$K = \overline{A + B}$$

A	B	K
0	0	1
0	1	0
1	0	0
1	1	0

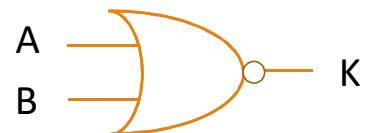

Expression

Truth table

Schematic



FACULDADE DE
CIÊNCIAS E TECNOLOGIA
UNIVERSIDADE NOVA DE LISBOA




CTS - Centre of Technology and Systems



LUÍS GOMES, 2014,15

Equivalent representations

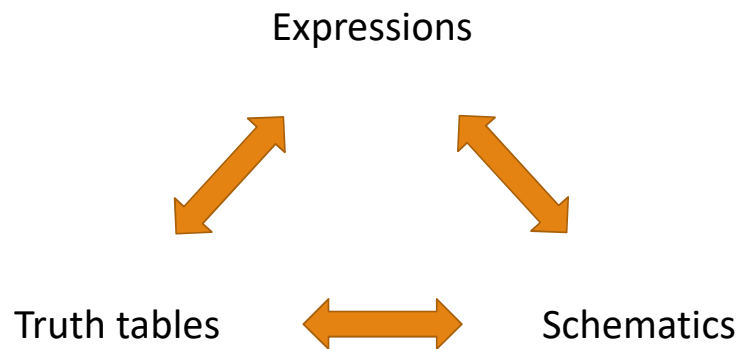


Describing a function

$$K = A + B.C$$

Expression

A	B	C	K
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

Truth table

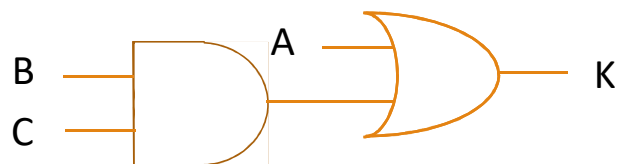

Schematic


Sixteen functions of two variables

A	B	f_0	f_1	f_2	f_3	f_4	f_5	f_6	f_7	f_8	f_9	f_{10}	f_{11}	f_{12}	f_{13}	f_{14}	f_{15}
0	0	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1
0	1	0	0	1	1	0	0	1	1	0	0	1	1	0	0	1	1
1	0	0	0	0	0	1	1	1	1	0	0	0	0	1	1	1	1
1	1	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1


Sixteen functions of two variables

A	B	f_0	f_1	f_2	f_3	f_4	f_5	f_6	f_7	f_8	f_9	f_{10}	f_{11}	f_{12}	f_{13}	f_{14}	f_{15}
0	0	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1
0	1	0	0	1	1	0	0	1	1	0	0	1	1	0	0	1	1
1	0	0	0	0	0	1	1	1	1	0	0	0	0	1	1	1	1
1	1	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1

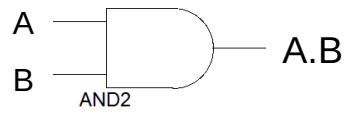
NOR → f_0
 NAND → f_6
 XOR → f_7
 XNOR → f_8
 INV → f_4
 AND → f_5
 OR → f_{15}



A	B	A.B
0	0	0
0	1	0
1	0	0
1	1	1

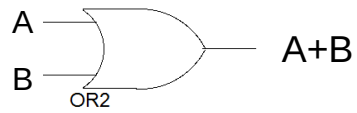


A	B	A+B
0	0	0
0	1	1
1	0	1
1	1	1

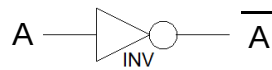


A	$\overline{A}$
0	1
1	0

LUÍS GOMES, 2014,15

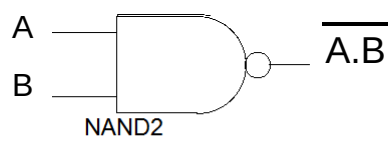


A	B	A.B	$\overline{A.B}$
0	0	0	1
0	1	0	1
1	0	0	1
1	1	1	0

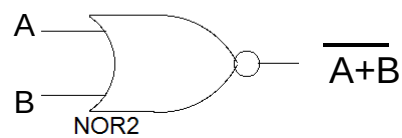


A	B	A+B	$\overline{A+B}$
0	0	0	1
0	1	1	0
1	0	1	0
1	1	1	0

LUÍS GOMES, 2014,15

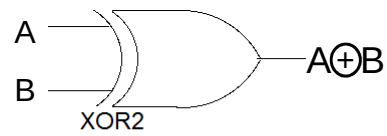


A	B	$A \oplus B$
0	0	0
0	1	1
1	0	1
1	1	0

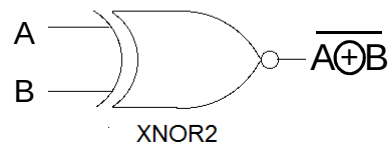

A	B	$\overline{A \oplus B}$
0	0	1
0	1	0
1	0	0
1	1	1


LUÍS GOMES, 2014,15

Standart schematic symbols

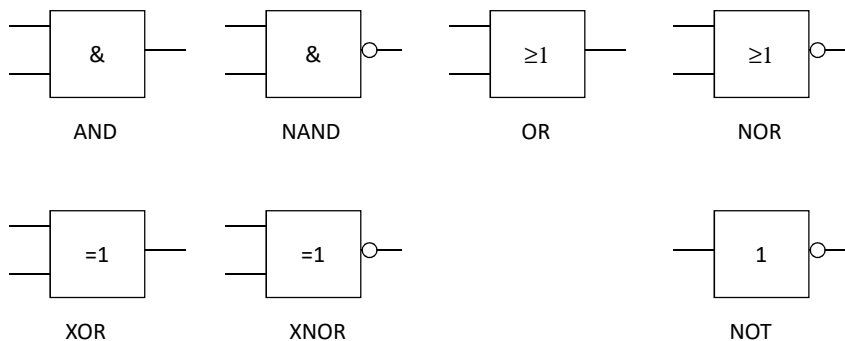

LUÍS GOMES, 2014,15

More on schematic symbols

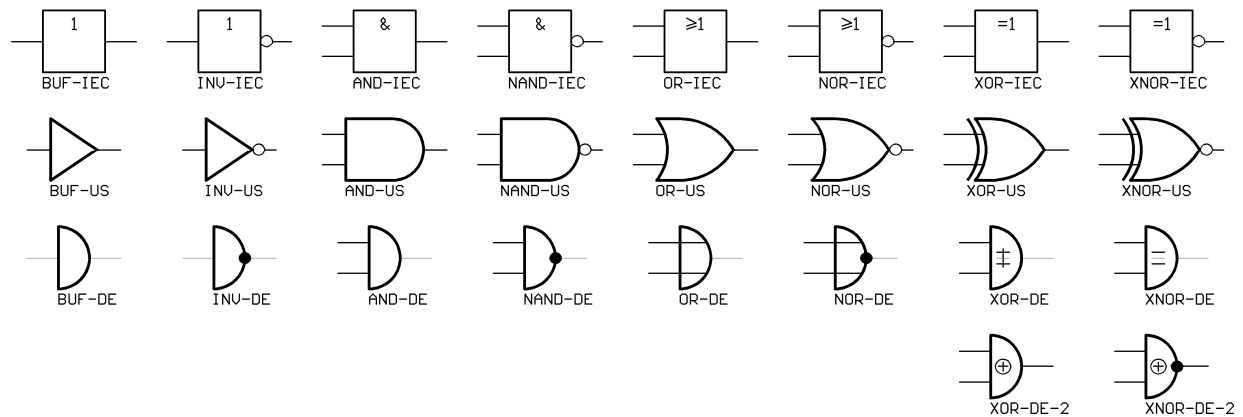

Basic postulates and theorems

$$A + B = B + A \quad A \cdot B = B \cdot A \quad (\text{commutative})$$

$$A + B + C = (A + B) + C = A + (B + C) \quad (\text{associative})$$

$$A \cdot B \cdot C = (A \cdot B) \cdot C = A \cdot (B \cdot C)$$

$$A \cdot (B + C) = A \cdot B + A \cdot C \quad (\text{distributive})$$

$$A + B \cdot C = (A + B) \cdot (A + C)$$

$$A + A \cdot B = A \quad A \cdot (A + B) = A \quad (\text{absorption})$$

DeMorgan's theorems

$$\overline{A \cdot B} = \overline{A} + \overline{B}$$

$$\overline{A + B} = \overline{A} \cdot \overline{B}$$

More basic theorems

$$A + \overline{A}.B = A + B$$

$$A . (\overline{A} + B) = A.B$$

$$A.B + A.\overline{B} = A$$

$$(A + B).(A + \overline{B}) = A$$

$$A.B + A.\overline{B}.C = A.B + A.C$$

$$(A+B).(A+\overline{B}+C) = (A+B) . (A+C)$$

$$A.B + \overline{A}.C + B.C = A.B + \overline{A}.C \quad (\text{consensus})$$

$$(A+B).(\overline{A}+C).(B+C) = (A+B).(\overline{A}+C)$$

Some postulates and theorems

DeMorgan's laws

$$\overline{A . B} = \overline{A} + \overline{B}$$

$$\overline{A + B} = \overline{A} . \overline{B}$$

$$(1) \overline{\overline{A} . \overline{B}} = \overline{\overline{A}} + \overline{\overline{B}}$$

$$(2) \overline{\overline{A} + \overline{B}} = \overline{\overline{A}} . \overline{\overline{B}}$$

$$(3) A = \overline{\overline{A}}$$

$$(4) A + A = A$$

$$(5) A . A = A$$

$$(6) A + 0 = A$$

$$(7) A . 1 = A$$

$$A = \overline{\overline{A}} \quad (\text{involution})$$

$$A + A = A$$

$$A . A = A$$

$$A + 0 = A \quad (\text{neutral})$$

$$A . 1 = A$$

OR+NOT or AND+NOT are sufficient

$$A \cdot B = \overline{\overline{A \cdot B}} = \overline{\overline{A} + \overline{B}}$$

$$A + B = \overline{\overline{A + B}} = \overline{\overline{A} \cdot \overline{B}}$$

$$(1) \overline{\overline{A \cdot B}} = \overline{\overline{A} + \overline{B}}$$

$$(2) \overline{\overline{A + B}} = \overline{\overline{A} \cdot \overline{B}}$$

$$(3) A = \overline{\overline{A}}$$

$$(4) A + A = A$$

$$(5) A \cdot A = A$$

$$(6) A + 0 = A$$

$$(7) A \cdot 1 = A$$

NORs are sufficient

$$A \cdot B = \overline{\overline{A \cdot B}} = \overline{\overline{A} + \overline{B}} = \overline{\overline{A + A} + \overline{B + B}}$$

$$A + B = \overline{\overline{A + B}} = \overline{\overline{A + B} + 0} = \overline{\overline{A + B} + \overline{\overline{A + B}}}$$

$$\overline{A} = \overline{A + A}$$

$$(1) \overline{\overline{A \cdot B}} = \overline{\overline{A} + \overline{B}}$$

$$(2) \overline{\overline{A + B}} = \overline{\overline{A} \cdot \overline{B}}$$

$$(3) A = \overline{\overline{A}}$$

$$(4) A + A = A$$

$$(5) A \cdot A = A$$

$$(6) A + 0 = A$$

$$(7) A \cdot 1 = A$$

NANDs are sufficient

$$A+B = \overline{\overline{A+B}} = \overline{\overline{A} \cdot \overline{B}} = \overline{\overline{A} \cdot \overline{A} \cdot \overline{B} \cdot \overline{B}}$$

$$A \cdot B = \overline{\overline{A \cdot B}} = \overline{\overline{A} \cdot \overline{B} \cdot 1} = \overline{\overline{A} \cdot \overline{B} \cdot \overline{\overline{A} \cdot \overline{B}}}$$

$$\overline{A} = \overline{A \cdot A}$$

$$(1) \overline{A \cdot B} = \overline{A} + \overline{B}$$

$$(2) \overline{A + B} = \overline{A} \cdot \overline{B}$$

$$(3) A = \overline{\overline{A}}$$

$$(4) A + A = A$$

$$(5) A \cdot A = A$$

$$(6) A + 0 = A$$

$$(7) A \cdot 1 = A$$

Using only NANDs

$$A \cdot B \cdot C + A \cdot D = \overline{\overline{A \cdot B \cdot C + A \cdot D}} = \overline{\overline{A \cdot B \cdot C} \cdot \overline{A \cdot D}}$$

$$(1) \overline{A \cdot B} = \overline{A} + \overline{B}$$

$$(2) \overline{A + B} = \overline{A} \cdot \overline{B}$$

$$(3) A = \overline{\overline{A}}$$

$$(4) A + A = A$$

$$(5) A \cdot A = A$$

$$(6) A + 0 = A$$

$$(7) A \cdot 1 = A$$

Using only 2-input NANDs

$$\begin{aligned}
 A.B.C + A.D &= \overline{\overline{A.B.C} + \overline{A.D}} = \overline{\overline{A.B.C} . \overline{A.D}} = \\
 &= \overline{\overline{A.B.C} . \overline{A.D}} = \overline{\overline{A.B} . \overline{A.B} . C . \overline{A.D}}
 \end{aligned}$$

Diagram illustrating the implementation of the expression $A.B.C + A.D$ using only 2-input NAND gates. The expression is transformed into a form that can be implemented using NAND gates. The steps are indicated by blue arrows with numbers:

- Step 3: $\overline{\overline{A.B.C} + \overline{A.D}}$ to $\overline{\overline{A.B.C} . \overline{A.D}}$
- Step 2: $\overline{\overline{A.B.C} . \overline{A.D}}$ to $\overline{\overline{A.B} . \overline{A.B} . C . \overline{A.D}}$
- Step 3: $\overline{\overline{A.B} . \overline{A.B} . C . \overline{A.D}}$ to $\overline{\overline{A.B} . \overline{A.B} . C . \overline{A.D}}$
- Step 5: $\overline{\overline{A.B} . \overline{A.B} . C . \overline{A.D}}$ to $\overline{\overline{A.B} . \overline{A.B} . C . \overline{A.D}}$

$$(1) \overline{A} . \overline{B} = \overline{A + B}$$

$$(2) \overline{A + B} = \overline{A} . \overline{B}$$

$$(3) A = \overline{\overline{A}}$$

$$(4) A + A = A$$

$$(5) A . A = A$$

$$(6) A + 0 = A$$

$$(7) A . 1 = A$$

Using only NORs

$$\begin{aligned}
 A.B.C + A.D &= \overline{\overline{A.B.C} + \overline{A.D}} = \overline{\overline{A+B+C} + \overline{A+D}} = \\
 &= \overline{\overline{A+A} + \overline{B+B} + \overline{C+C} + \overline{A+A} + \overline{D+D} + 0}
 \end{aligned}$$

Diagram illustrating the implementation of the expression $A.B.C + A.D$ using only 2-input NOR gates. The expression is transformed into a form that can be implemented using NOR gates. The steps are indicated by blue arrows with numbers:

- Step 3: $\overline{\overline{A.B.C} + \overline{A.D}}$ to $\overline{\overline{A+B+C} + \overline{A+D}}$
- Step 1: $\overline{\overline{A+B+C} + \overline{A+D}}$ to $\overline{\overline{A+A} + \overline{B+B} + \overline{C+C} + \overline{A+A} + \overline{D+D} + 0}$
- Step 4+6: $\overline{\overline{A+A} + \overline{B+B} + \overline{C+C} + \overline{A+A} + \overline{D+D} + 0}$ to $\overline{\overline{A+A} + \overline{B+B} + \overline{C+C} + \overline{A+A} + \overline{D+D} + 0}$

$$(1) \overline{A} . \overline{B} = \overline{A + B}$$

$$(2) \overline{A + B} = \overline{A} . \overline{B}$$

$$(3) A = \overline{\overline{A}}$$

$$(4) A + A = A$$

$$(5) A . A = A$$

$$(6) A + 0 = A$$

$$(7) A . 1 = A$$

Digital systems: from bits to microcontrollers

- Introduction to digital systems fundamentals
- Combinatorial digital systems
- Sequential digital systems
- Introduction to microcontrollers
- Introduction to advanced implementation platforms



FACULDADE DE
CIÊNCIAS E TECNOLOGIA
UNIVERSIDADE NOVA DE LISBOA



CTS - Centre of Technology and Systems



LUÍS GOMES, 2014,15,16

Algebraic forms of functions

Two possible forms:

- SOP (sum of products) or
- POS (product of sums).

(sum = Oring product = ANDing)

Examples:

$$f_1(A,B,C) = A.B + B.C$$

$$f_2(A,B,C) = (A+B).(B+C)$$



FACULDADE DE
CIÊNCIAS E TECNOLOGIA
UNIVERSIDADE NOVA DE LISBOA



CTS - Centre of Technology and Systems



LUÍS GOMES, 2014,15

Canonical forms

Two possible forms:

- Canonical SOP (sum of minterms) or
- Canonical POS (product of maxterms).

(sum = Oring product = ANDing)

minterm = product containing all variables

maxterm = sum containing all variables

Defining minterms

		expression	
A	B	equiv.	2 variable function
0	0	$\overline{A}.\overline{B}$	m_0
0	1	$\overline{A}.B$	m_1
1	0	$A.\overline{B}$	m_2
1	1	$A.B$	m_3

4 variable function

minterm = product containing all variables
 0 → complemented variable
 1 → uncomplemented variable

A	B	C	D	
0	0	0	0	m_0
0	0	0	1	m_1
0	0	1	0	m_2
0	0	1	1	m_3
0	1	0	0	m_4
0	1	0	1	m_5
0	1	1	0	m_6
0	1	1	1	m_7
1	0	0	0	m_8
1	0	0	1	m_9
1	0	1	0	m_{10}
1	0	1	1	m_{11}
1	1	0	0	m_{12}
1	1	0	1	m_{13}
1	1	1	0	m_{14}
1	1	1	1	m_{15}

Defining a function using sum of minterms

		expression	
A	B	equiv.	
0	0	$\bar{A} \cdot \bar{B}$	m_0
0	1	$\bar{A} \cdot B$	m_1
1	0	$A \cdot \bar{B}$	m_2
1	1	$A \cdot B$	m_3

A	B	K
0	0	0
0	1	0
1	0	1
1	1	0

$$K = m_2 = \sum m(2)$$

$$K = A \cdot \bar{B}$$

2 variable function



LUÍS GOMES, 2014,15

Defining maxterms

		expression	
A	B	equiv.	
0	0	$A+B$	M_0
0	1	$A+\bar{B}$	M_1
1	0	$\bar{A}+B$	M_2
1	1	$\bar{A}+\bar{B}$	M_3

2 variable function

4 variable function

A	B	C	D	
0	0	0	0	M_0
0	0	0	1	M_1
0	0	1	0	M_2
0	0	1	1	M_3
0	1	0	0	M_4
0	1	0	1	M_5
0	1	1	0	M_6
0	1	1	1	M_7
1	0	0	0	M_8
1	0	0	1	M_9
1	0	1	0	M_{10}
1	0	1	1	M_{11}
1	1	0	0	M_{12}
1	1	0	1	M_{13}
1	1	1	0	M_{14}
1	1	1	1	M_{15}

maxterm = sum containing all variables
 0 → uncomplemented variable
 1 → complemented variable



LUÍS GOMES, 2014,15

Defining a function using product of maxterms

A	B	expression equiv.
0	0	M_0 $A+B$
0	1	M_1 $A+\bar{B}$
1	0	M_2 $\bar{A}+B$
1	1	M_3 $\bar{A}+\bar{B}$

A	B	K
0	0	0
0	1	0
1	0	1
1	1	0

$$K = M_0 \cdot M_1 \cdot M_3 = \prod M(0,1,3)$$

$$K = (A+B) \cdot (A+\bar{B}) \cdot (\bar{A}+\bar{B})$$

2 variable function



LUÍS GOMES, 2014,15

Defining a function using 1's and 0's

A	B	1's equiv.	0's equiv.
0	0	$\bar{A} \cdot \bar{B}$	$A+B$
0	1	$\bar{A} \cdot B$	$A+\bar{B}$
1	0	$A \cdot \bar{B}$	$\bar{A}+B$
1	1	$A \cdot B$	$\bar{A}+\bar{B}$

A	B	K
0	0	0
0	1	0
1	0	1
1	1	0

$$K = A \cdot \bar{B}$$

$$K = (A+B) \cdot (A+\bar{B}) \cdot (\bar{A}+\bar{B})$$



LUÍS GOMES, 2014,15

Defining a function using 1's and 0's

A	B	1's equiv.	0's equiv.
0	0	$\overline{A}.\overline{B}$	$A+B$
0	1	$\overline{A}.B$	$A+\overline{B}$
1	0	$A.\overline{B}$	$\overline{A}+B$
1	1	$A.B$	$\overline{A}+\overline{B}$

A	B	K
0	0	0
0	1	0
1	0	1
1	1	0

$$K = A . \overline{B}$$

$= ?$

$$K = (A+B).(A+\overline{B}).(\overline{A}+\overline{B})$$

$$\begin{aligned}
 K &= (A+B).(A+\overline{B}).(\overline{A}+\overline{B}) = (A.A+A.\overline{B}+A.B+B.\overline{B}).(\overline{A}+\overline{B}) = (A+A.(\overline{B}+B)+0).(\overline{A}+\overline{B}) = \\
 &= (A+A.1).(\overline{A}+\overline{B}) = (A+A).(\overline{A}+\overline{B}) = A.(\overline{A}+\overline{B}) = A.\overline{A}+A.\overline{B} = 0+A.\overline{B} = A.\overline{B}
 \end{aligned}$$

A	B	$A.\overline{B}$	$A+B$	$A+\overline{B}$	$\overline{A}+\overline{B}$	$(A+B).(A+\overline{B}).(\overline{A}+\overline{B})$
0	0	0	0	1	1	0
0	1	0	1	0	1	0
1	0	1	1	1	1	1
1	1	0	1	1	0	0

