

Digital systems: from bits to microcontrollers

- Introduction to digital systems fundamentals
- Combinatorial digital systems
- Sequential digital systems
- Introduction to microcontrollers
- Introduction to advanced implementation platforms



LUÍS GOMES, 2014,15,16,17

Number systems

- positional notation,
- decimal representation,
- binary representation,
- octal representation, and
- hexadecimal representation;
- conversions between bases



LUÍS GOMES, 2014,15

Positional notation

$$A = (\overbrace{a_{n-1}a_{n-2}\dots a_1a_0}^{\text{integer part}} \cdot \overbrace{a_{-1}a_{-2}\dots a_{-m}}^{\text{fractional part}})_r$$

↑ most significant digit ↑ least significant digit

radix

Polynomial notation

$$A = (a_{n-1}a_{n-2}\dots a_1a_0 \cdot a_{-1}a_{-2}\dots a_{-m})_r$$

$$A = a_{n-1} \cdot r^{n-1} + a_{n-2} \cdot r^{n-2} + \dots + a_1 \cdot r^1 + a_0 \cdot r^0 + a_{-1} \cdot r^{-1} + a_{-2} \cdot r^{-2} + \dots + a_{-m} \cdot r^{-m}$$

$$A = \sum_{i=-m}^{i=n-1} a_i \cdot r^i$$

DECIMAL

- Radix: 10 Symbols: 0,1,2,3,4,5,6,7,8,9
- $1357 \Rightarrow 1 \times 10^3 + 3 \times 10^2 + 5 \times 10^1 + 7 \times 10^0$

OCTAL

- Radix: 8 Symbols: 0,1,2,3,4,5,6,7
- $2615 \Rightarrow 2 \times 8^3 + 6 \times 8^2 + 1 \times 8^1 + 5 \times 8^0$

HEXADECIMAL


- Radix: 16 Symbols: 0,1,2,3,4,5,6,7,8,9,A,B,C,D,E,F
- $A05F \Rightarrow 10 \times 16^3 + 0 \times 16^2 + 5 \times 16^1 + 15 \times 16^0$

BINARY

- Radix: 2 Symbols: 0,1
- $1011 \Rightarrow 1 \times 2^3 + 0 \times 2^2 + 1 \times 2^1 + 1 \times 2^0$


LUÍS GOMES, 2014,15

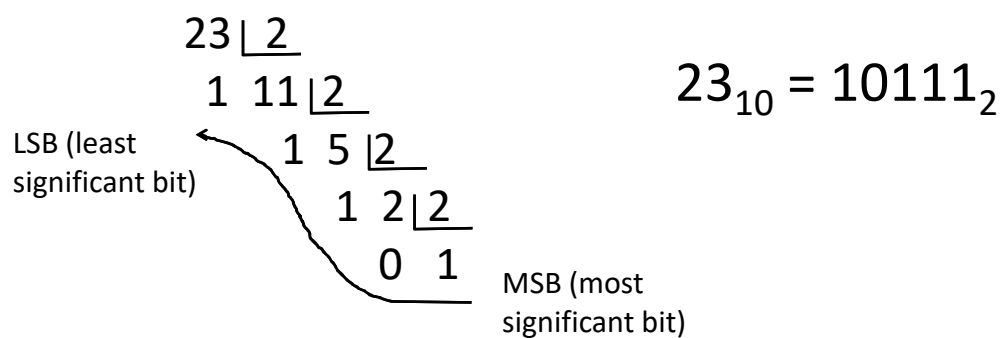Conversion from decimal to binary: integer part



LUÍS GOMES, 2014,15

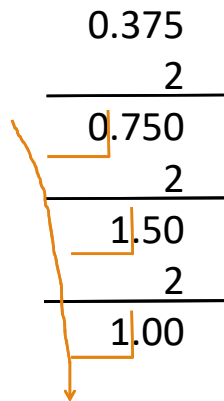Conversion from decimal to binary: fractional part



$$0.375_{10} = 0.011_2$$

Conversion from decimal to binary

integer part

$$23_{10} = 10111_2$$

$$23.375_{10} = 10111.011_2$$

$$0.375_{10} = 0.011_2$$

fractional part

Conversion from binary to decimal: integer part

$$\begin{aligned}
 10111_2 &= 1 \times 2^4 + 0 \times 2^3 + 1 \times 2^2 + 1 \times 2^1 + 1 \times 2^0 = \\
 &= 1 \times 16 + 0 \times 8 + 1 \times 4 + 1 \times 2 + 1 \times 1 = \\
 &= 16 + 4 + 2 + 1 = \\
 &= 23
 \end{aligned}$$

$$10111_2 = 23_{10}$$

Conversion from binary to decimal: integer part

$$\begin{aligned}
 10111_2 &= 1 \times 2^4 + 0 \times 2^3 + 1 \times 2^2 + 1 \times 2^1 + 1 \times 2^0 = \\
 &\quad \swarrow \quad \searrow \quad \swarrow \quad \searrow \quad \swarrow \quad \searrow \\
 &= 16 + 4 + 2 + 1 = \\
 &= 23
 \end{aligned}$$

$$10111_2 = 23_{10}$$

Conversion from binary to decimal: fractional part

$$\begin{aligned}
 0.101_2 &= 1 \times 2^{-1} + 0 \times 2^{-2} + 1 \times 2^{-3} = \\
 &= 1 \times 0.5 + 0 \times 0.25 + 1 \times 0.125 = \\
 &= 0.5 + 0.125 = \\
 &= 0.625
 \end{aligned}$$

$$0.101_2 = 0.625_{10}$$

Conversion from binary to decimal: fractional part

$$\begin{aligned}
 0.101_2 &= 1 \times 2^{-1} + 0 \times 2^{-2} + 1 \times 2^{-3} = \\
 &\quad \swarrow \quad \searrow \\
 &= 0.5 + 0.125 = \\
 &= 0.625
 \end{aligned}$$

$$0.101_2 = 0.625_{10}$$

Conversion from binary to decimal

$$\begin{aligned}
 10111.101_2 &= 1 \times 2^4 + 0 \times 2^3 + 1 \times 2^2 + 1 \times 2^1 + 1 \times 2^0 + 1 \times 2^{-1} + 0 \times 2^{-2} + 1 \times 2^{-3} = \\
 &= 16 + 4 + 2 + 1 + 0.5 + 0.125 = \\
 &= 23.625
 \end{aligned}$$

$$10111.101_2 = 23.625_{10}$$

Converting binary to/from octal

Power of two radix can be easily converted to/from binary!

Octal $\rightarrow$ 1 octal digit = 3 binary digit

$$\begin{array}{ccc}
 2 & 7 & 5 \\
 \text{---} & \text{---} & \text{---} \\
 10111.101_2 & = & 27.5_8
 \end{array}$$

Binary	Octal
0 0 0	0
0 0 1	1
0 1 0	2
0 1 1	3
1 0 0	4
1 0 1	5
1 1 0	6
1 1 1	7

Converting binary to/from hexadecimal

Hexadecimal $\rightarrow$ 1 hexadecimal digit = 4 binary digit

$$\begin{array}{c} \text{1} \quad \text{7} \quad \text{A} \\ \hline 10111.101_2 = 17.A_{16} \end{array}$$

Binary	Hex	Binary	Hex
0000	0	1000	8
0001	1	1001	9
0010	2	1010	A
0011	3	1011	B
0100	4	1100	C
0101	5	1101	D
0110	6	1110	E
0111	7	1111	F

Converting numbers

$$10111.101_2 = 27.5_8 = 23.625_{10} = 17.A_{16}$$

Higher radix $\rightarrow$ Lower number of digits (compact representation)

Counting in different number systems

Decimal Binary Octal Hex

0	0	0	0
1	1	1	1
2	10	2	2
3	11	3	3
4	100	4	4
5	101	5	5
6	110	6	6
7	111	7	7

Decimal Binary Octal Hex

8	1000	10	8
9	1001	11	9
10	1010	12	A
11	1011	13	B
12	1100	14	C
13	1101	15	D
14	1110	16	E
15	1111	17	F
16	10000	20	10

Major goal for next steps

Illustrate how modular composition/decomposition is important in system design to suport top-down and bottom-up approaches.

Different types of combinatorial modules will be used to illustrate the concept.

Potential impact on several aspects will be analysed (ranging from costs and power consumption to performance)

Data representation

Numerical data

Alphanumeric data (example: ASCII)



Different types of codes and coding strategies

Natural Binary Code (using 4 bits)

Decimal Value	Natural Binary	Decimal Value	Natural Binary
0	0 0 0 0	8	1 0 0 0
1	0 0 0 1	9	1 0 0 1
2	0 0 1 0	10	1 0 1 0
3	0 0 1 1	11	1 0 1 1
4	0 1 0 0	12	1 1 0 0
5	0 1 0 1	13	1 1 0 1
6	0 1 1 0	14	1 1 1 0
7	0 1 1 1	15	1 1 1 1

Gray Code (using 3 bits)

Value	Natural Binary	Gray	Decimal Value
0	000	000	0
1	001	001	1
2	010	011	3
3	011	010	2
4	100	110	6
5	101	111	7
6	110	101	5
7	111	100	4

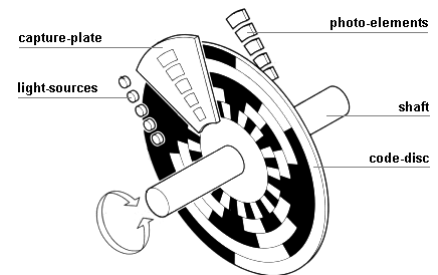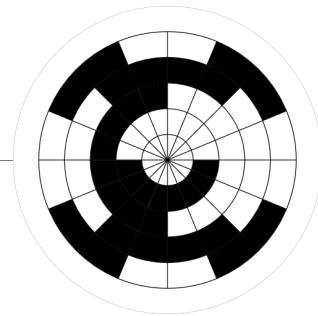


LUÍS GOMES, 2014,15

Binary decimal codes

Maybe the most well known binary decimal codes are:

- BCD8421
- 2 out-of 5

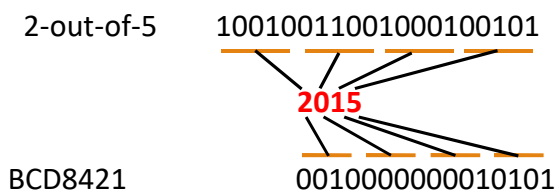

BCD 8421		2 out-of 5 P '7' '4' '2' '1'
0000	0	01100
0001	1	10001
0010	2	10010
0011	3	00011
0100	4	10100
0101	5	00101
0110	6	00110
0111	7	11000
1000	8	01001
1001	9	01010



Decoders

An n -to- 2^n decoder is a combinatorial circuit with n input lines and 2^n output signals, which one decoding one minterm of the input lines.

Example of a 2-to-4 decoder:


A_1	A_0	O_0	O_1	O_2	O_3
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

$$O_0 = f_0(A_1, A_0) = m_0 = \neg A_1 \cdot \neg A_0$$

$$O_1 = f_1(A_1, A_0) = m_1 = \neg A_1 \cdot A_0$$

$$O_2 = f_2(A_1, A_0) = m_2 = A_1 \cdot \neg A_0$$
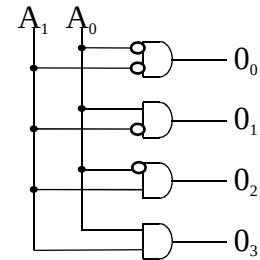
$$O_3 = f_3(A_1, A_0) = m_3 = A_1 \cdot A_0$$



Decoders

Example of a 3-to-8 decoder:

A_2	A_1	A_0	O_0	O_1	O_2	O_3	O_4	O_5	O_6	O_7
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1

$$O_0 = f_0(A_2, A_1, A_0) = m_0 = \neg A_2 \cdot \neg A_1 \cdot \neg A_0$$

$$O_1 = f_1(A_2, A_1, A_0) = m_1 = \neg A_2 \cdot \neg A_1 \cdot A_0$$

$$O_2 = f_2(A_2, A_1, A_0) = m_2 = \neg A_2 \cdot A_1 \cdot \neg A_0$$

$$O_3 = f_3(A_2, A_1, A_0) = m_3 = \neg A_2 \cdot A_1 \cdot A_0$$

$$O_4 = f_4(A_2, A_1, A_0) = m_4 = A_2 \cdot \neg A_1 \cdot \neg A_0$$


$$O_5 = f_5(A_2, A_1, A_0) = m_5 = A_2 \cdot \neg A_1 \cdot A_0$$

$$O_6 = f_6(A_2, A_1, A_0) = m_6 = A_2 \cdot A_1 \cdot \neg A_0$$

$$O_7 = f_7(A_2, A_1, A_0) = m_7 = A_2 \cdot A_1 \cdot A_0$$

Decimal decoders

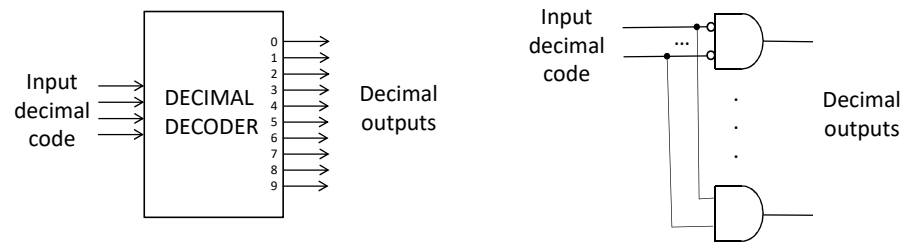A decimal decoder is a combinatorial circuit receiving a decimal binary code and producing 10 output signals, each one decoding one decimal code presented in the input.




Implementation of combinatorial functions using decoders

A_1	A_0	O_0	O_1	O_2	O_3
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

X	Y	Z
0	0	0
0	1	1
1	0	1
1	1	0

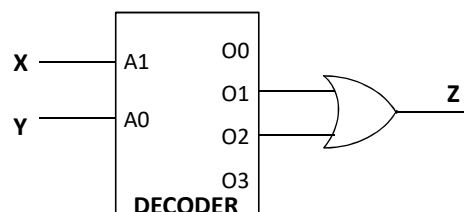
$$Z(X,Y) = \Sigma(1,2) \equiv O_1 + O_2$$



Implementation of combinatorial functions using decoders

$$Z(X,Y,W) = \Sigma(5,6,7) \equiv O5 + O6 + O7$$

	X	Y	W	Z
0	0	0	0	0
1	0	0	1	0
2	0	1	0	0
3	0	1	1	0
4	1	0	0	0
5	1	0	1	1
6	1	1	0	1
7	1	1	1	1

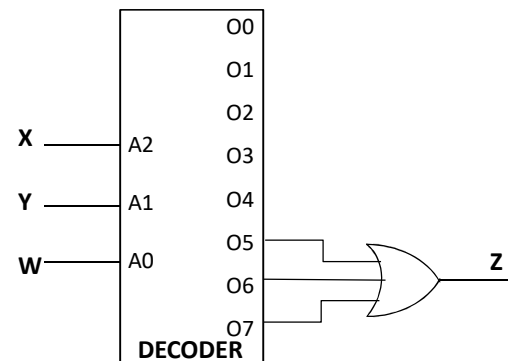


LUÍS GOMES, 2014,15


Implementation of combinatorial functions using decoders

$$Z(X,Y,W) = \Sigma(5,6,7)$$

	X	Y	W	Z
0	0	0	0	0
1	0	0	1	0
2	0	1	0	0
3	0	1	1	0
4	1	0	0	0
5	1	0	1	1
6	1	1	0	1
7	1	1	1	1

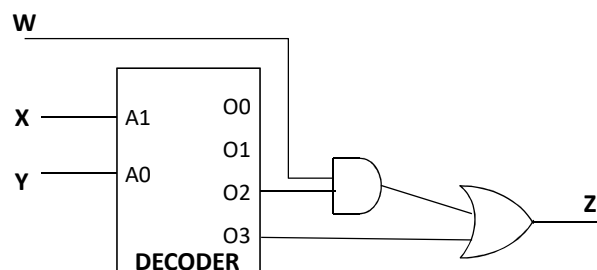

$$Z(X,Y,W) = O5 + O6 + O7$$

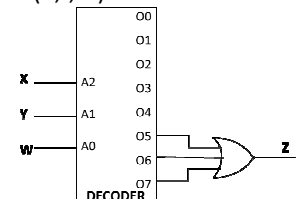


LUÍS GOMES, 2014,15

Implementation of combinatorial functions using decoders

$$Z(X,Y,W) = \Sigma(5,6,7)$$


	X	Y	W	Z
0	0	0	0	0
1	0	0	1	0
2	0	1	0	0
3	0	1	1	0
4	1	0	0	0
5	1	0	1	1
6	1	1	0	1
7	1	1	1	1

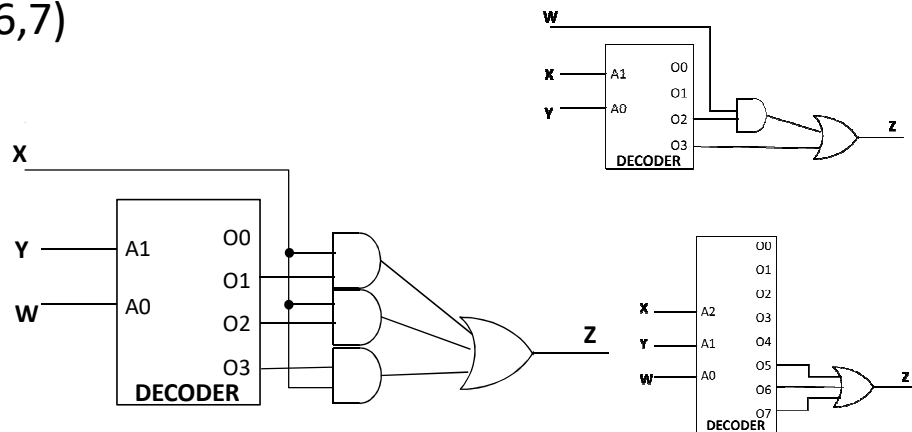

Encoder

An encoder is a combinatorial circuit generating a unique code on its outputs associated with each input signal.

Example: BCD encoder

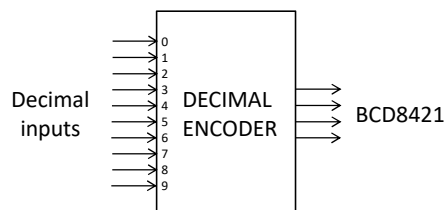


Encoding into 2-bit natural binary

I_3	I_2	I_1	I_0	A_1	A_0
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1


$$A_1 = I_3 + I_2$$

$$A_0 = I_3 + I_1$$

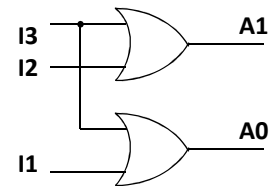




Considering that at least one input is active and only one input is active at a time

Converting codes: from 2 out-of-5 to BCD

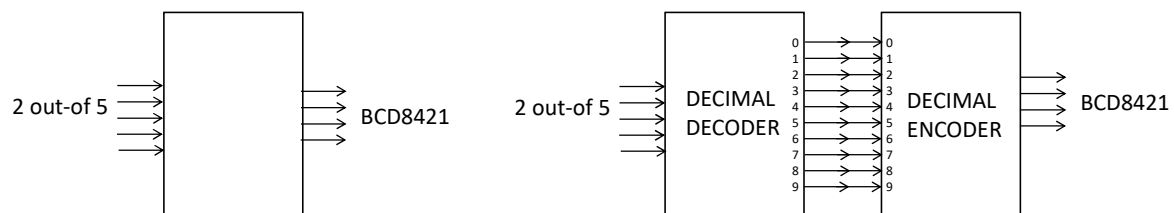

Converting codes: from natural binary to Gray (using 3 bits)

Natural Binary	$B_2 B_1 B_0$	$G_2 G_1 G_0$ Gray
0	000	000
1	001	001
2	010	011
3	011	010
4	100	110
5	101	111
6	110	101
7	111	100

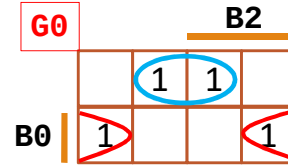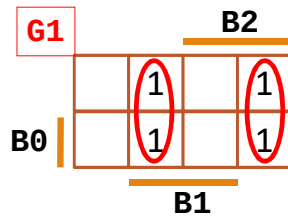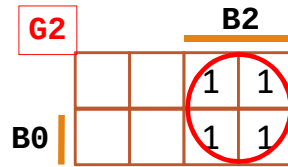


$$G2 = B2$$


$$G1 = B2 \cdot B1 + B2 \cdot \overline{B1} = B2 \oplus B1$$

$$G0 = B1 \cdot B0 + \overline{B1} \cdot B0 = B1 \oplus B0$$

Introducing an enable input

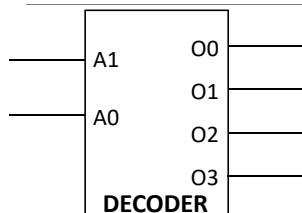


A_1	A_0	O_0	O_1	O_2	O_3
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

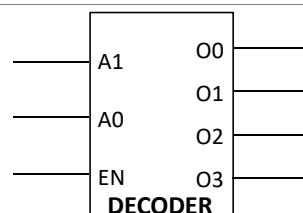


EN	A_1	A_0	O_0	O_1	O_2	O_3
0	x	x	0	0	0	0
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1

Active at 1 or active at 0 ?

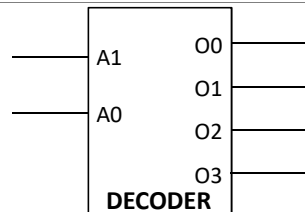


A ₁	A ₀	O ₀	O ₁	O ₂	O ₃
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

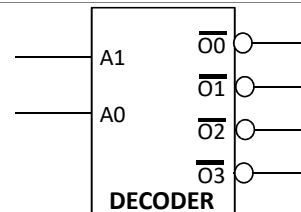


A ₁	A ₀	$\overline{O_0}$	$\overline{O_1}$	$\overline{O_2}$	$\overline{O_3}$
0	0	0	1	1	1
0	1	1	0	1	1
1	0	1	1	0	1
1	1	1	1	1	0

Active at 1 or active at 0 ?

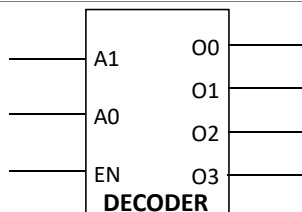

EN	A ₁	A ₀	O ₀	O ₁	O ₂	O ₃
0	x	x	0	0	0	0
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1

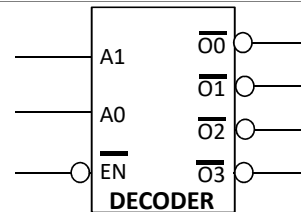

$\overline{EN}$	A ₁	A ₀	$\overline{O_0}$	$\overline{O_1}$	$\overline{O_2}$	$\overline{O_3}$
1	x	x	1	1	1	1
0	0	0	0	1	1	1
0	0	1	1	0	1	1
0	1	0	1	1	0	1
0	1	1	1	1	1	0