
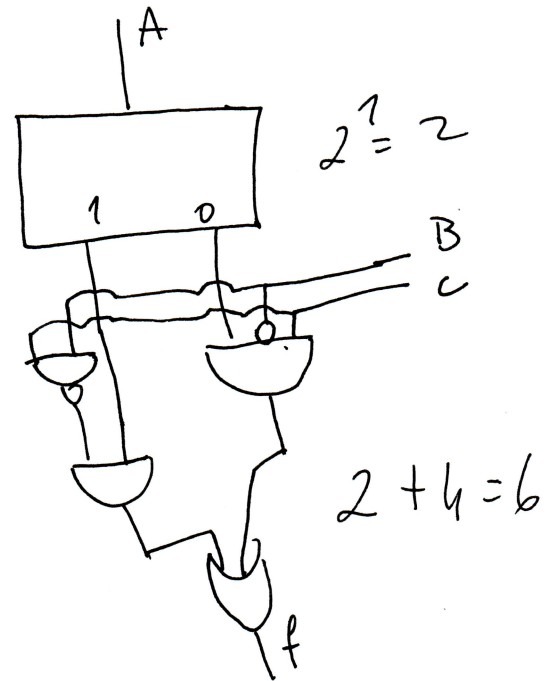
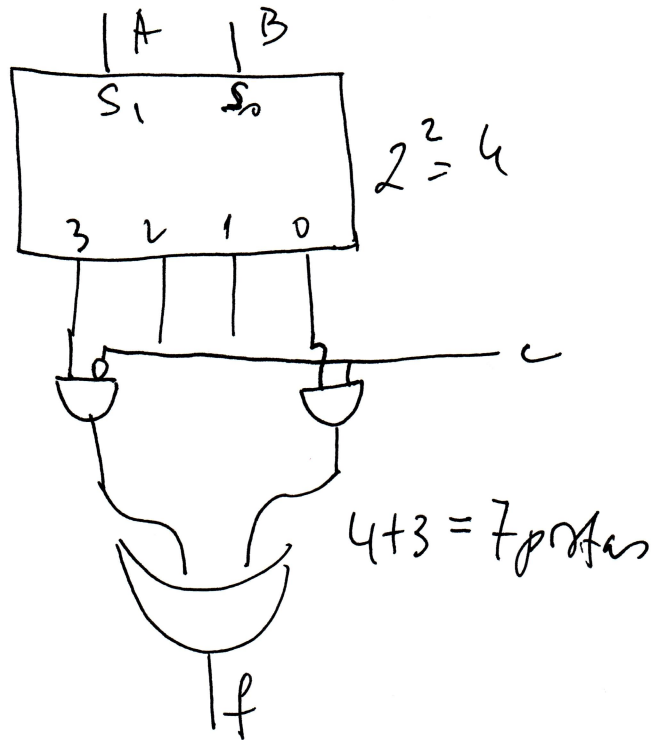


Q1
a)

A	B	C	D	E
0	0	0	0	0
0	0	0	1	1
0	0	1	0	0
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	0
0	1	1	1	1
1	0	0	0	1
1	0	0	1	0
1	0	1	0	1
1	0	1	1	0
1	1	0	0	1
1	1	0	1	0
1	1	1	0	1
1	1	1	1	0

Q₁ $F(A,B,C) = \prod(0,2,3,7)$

AB\c	0	1	
00	0	1	C
01	0	0	0
10	1	1	1
11	1	0	$\bar{C}$

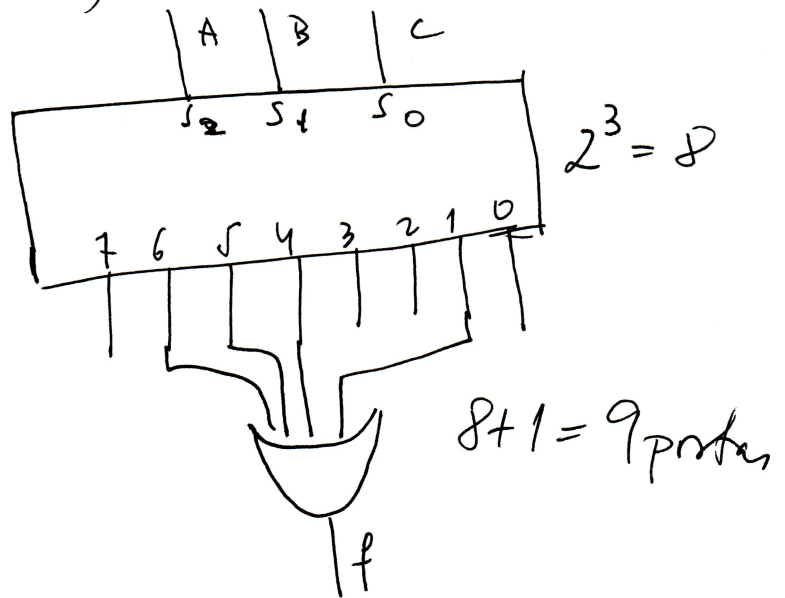

a melhor solução é
com decodificador
de uma variável

A = 0 $\bar{B}C$

B \ C	0	1
0	0	0
1	1	0

A = 1 $\bar{B} + \bar{C}$

B \ C	0	1
0	1	1
1	1	0

$\overline{BC}$

$$Q_1$$

$$c) F = A * (B + [C_1 C_0]) + D$$

$$\begin{array}{r}
 B \\
 + C_1 C_0 \\
 \hline
 S_2' S_1' S_0' \neq A \\
 \hline
 A S_2' A S_1' A S_0' \\
 + D \\
 \hline
 S_2 S_1 S_0
 \end{array}$$

podemos utilizar unicamente
semi somadores

Porque nunca temos
de somar 3 bits

(dois bit do número mais
o transporte da soma
anterior)

$$S_2 = AS_2 \text{ ou } T_1$$

Porque

1) se $C_1 C_0 = 11$
e $B = 1$
e $A = 1$
e $D = 1$
então


$$\begin{array}{r}
 A S_2' A S_1' A S_0' \\
 1 \quad 0 \quad 0 \\
 \hline
 1 \\
 \hline
 1 \quad 0 \quad 1
 \end{array}$$

para todos os outros
casos $AS_2' = 0$

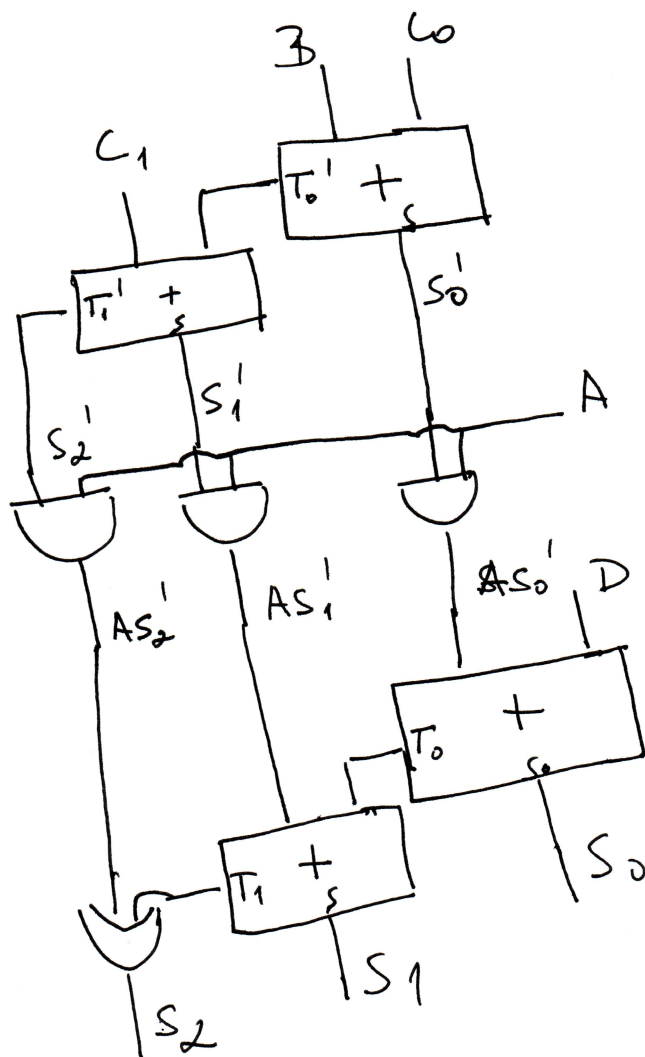2) considerando

$AS_1' = 1$ e $AS_0' = 1$
e $D = 1$


$$\begin{array}{r}
 1 \quad 1 \\
 + 1 \\
 \hline
 T_1 \quad 0 S_1 \quad 0 S_0
 \end{array}$$



$$T_1 = 1$$

para todos os outros
casos $T_1 = 0$

Q₁
d) Detectar 00 ou 11 com sobreposição

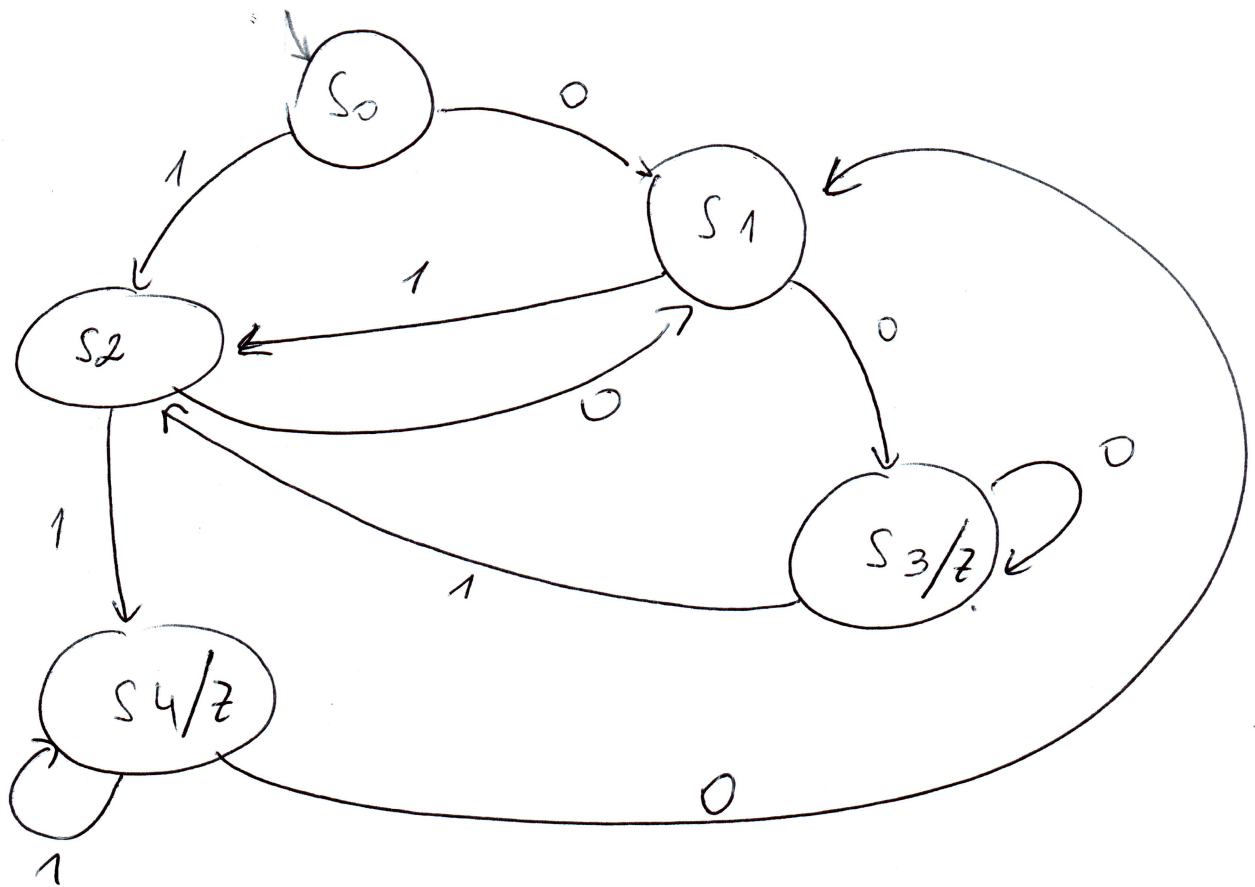

Q_2

a)

$R Q_2 Q_1 Q_0$	$D_2 D_1 D_0$ $Q_2 Q_1 Q_0$
0 0 0 0	1 0 0
0 0 0 1	0 1 1
0 0 1 0	0 0 1
0 0 1 1	1 1 0

0 1 0 0	0 1 0
0 1 0 1	X X X
0 1 1 0	0 0 0
0 1 1 1	X X X

1 0 0 0	0 0 0
1 0 0 1	0 0 0
1 0 1 0	0 0 0
1 0 1 1	0 0 0

1 1 0 0	0 0 0
1 1 0 1	X X X
1 1 1 0	0 0 0
1 1 1 1	X X X

$R Q_2 Q_1 Q_0$	0 0	0 1	1 1	1 0
0 0	1	0	0	0
0 1	0	X	X	0
1 1	1	X	X	0
1 0	0	0	0	0

$$D_2 = \overline{R} \overline{Q_2} \overline{Q_1} \overline{Q_0} + \overline{R} Q_1 Q_0$$

$R Q_2 Q_1 Q_0$	0 0	0 1	1 1	1 0
0 0	0	1	0	0
0 1	1	X	X	0
1 1	1	X	X	0
1 0	0	0	0	0

$$D_1 = \overline{R} Q_0 + \overline{R} Q_2 Q_1$$

$R Q_2 Q_1 Q_0$	0 0	0 1	1 1	1 0
0 0	0	0	0	0
0 1	1	X	X	0
1 1	0	X	X	0
1 0	1	0	0	0

$$D_0 = \overline{R} \overline{Q_2} Q_1 \overline{Q_0} + \overline{R} \overline{Q_1} Q_0$$

c) Substituindo

nas expressões

$$Q_2 = 1; Q_1 = 1; Q_0 = 1; R = 0$$

$$D_2 = \overline{0} \overline{1} \overline{1} \overline{1} + \overline{0} 1 1 = 1$$

$$D_1 = \overline{0} 1 + \overline{0} \overline{1} 1 = 1$$

$$D_0 = \overline{0} \overline{1} 1 \overline{1} + \overline{0} \overline{1} 1 = 0$$

Próximo estado MO (6)

$$Q_2 = 1; Q_1 = 1; Q_0 = 1; R = 1$$

$$D_2 = \overline{1} \overline{1} \overline{1} \overline{1} + \overline{1} 1 1 = 0 \quad D_0 = \overline{1} \overline{1} \overline{1} 1 + \overline{1} \overline{1} 1 = 0$$

$$D_1 = \overline{1} 1 + \overline{1} \overline{1} 1 = 0 \quad \text{Próximo estado } 000 (0)$$