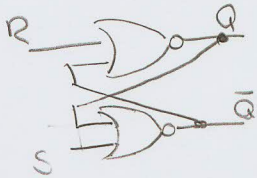


$\bar{S}$	$\bar{R}$	Q_{n+1}
0	0	X
0	1	1
1	0	0
1	1	Q



R	S	Q_{n+1}
0	0	Q
0	1	1
1	0	0
1	1	$\bar{Q}$




FLIP-FLOP

MASTER-SLAVE


EDGE-TRIGGERED

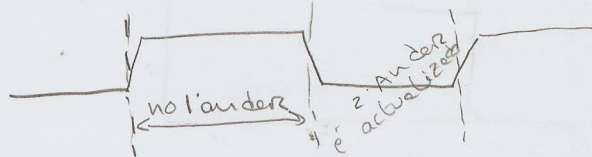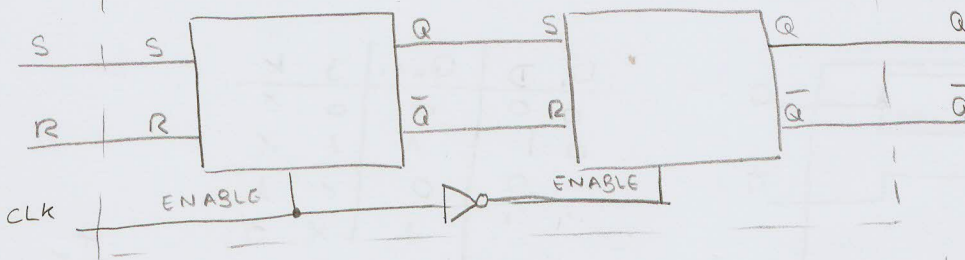

FLIP-FLOP D

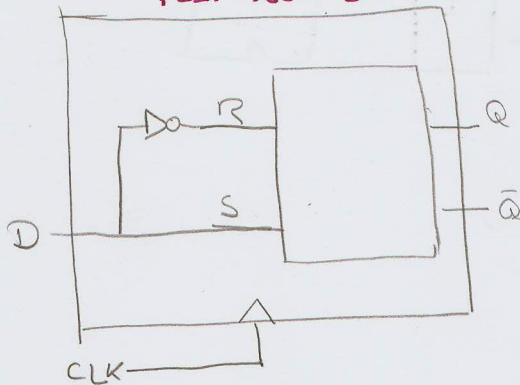

D	Q_{n+1}
0	0
1	1

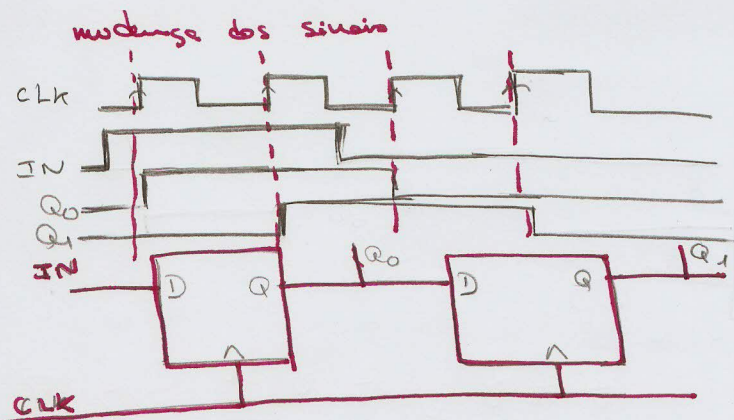

Q_1 atrasado no tempo em relação a Q_0

Registro de deslocamento

função do flip flop D: passo a informação.


D de Delay

3 Tipos de flip flop


J	K	Q_{n+1}
0	0	Q_n
0	1	0
1	0	1
1	1	$\bar{Q}_n$

T	Q_{n+1}
0	Q_n
1	$\bar{Q}_n$

D	Q_{n+1}
0	0
1	1

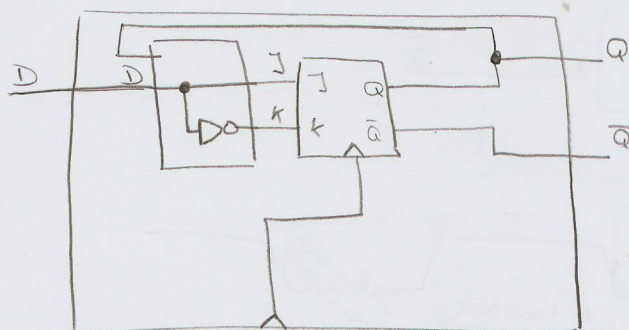

Q_n, D	Q_{n+1}	J	K
0 0	0	0	x
0 1	1	1	x
1 0	0	x	1
1 1	1	x	0

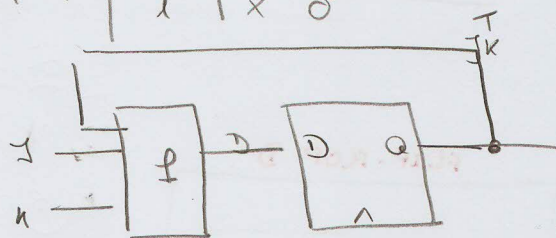

$Q_n \rightarrow Q_{n+1}$	J	K	D	T
0 $\rightarrow$ 0	0	x	0	0
0 $\rightarrow$ 1	1	x	1	1
1 $\rightarrow$ 0	x	1	0	1
1 $\rightarrow$ 1	x	0	1	0

(J)

Q_n	$\bar{Q}_n$
0	x
1	x

$J = D$

(K)

Q_n	$\bar{Q}_n$
x	1
x	

$K = \bar{D}$